
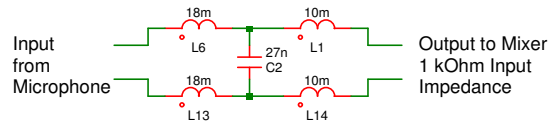


3rd Order, 8 kHz, -35 dB @ 25 kHz


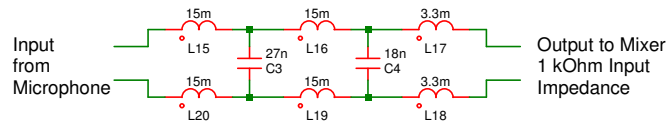


5th Order, 9 kHz, -47 dB @ 25 kHz




Simulation Circuits:

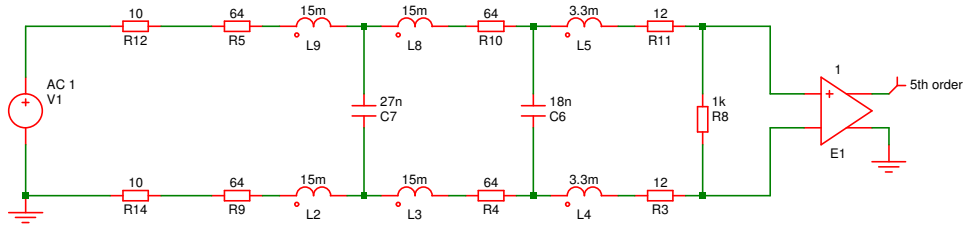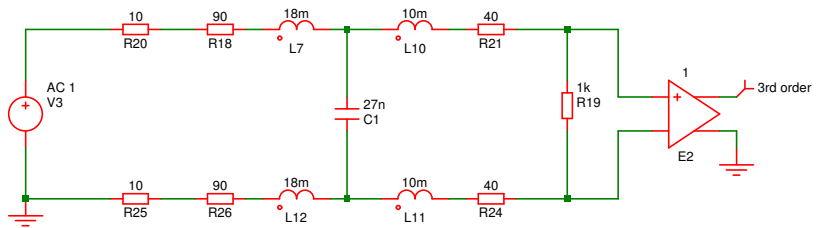(10 Ohm: Source impedance, 1 kOhm: Sink (mixer) impedance, others: Inductor's parasitic resistances)



dB

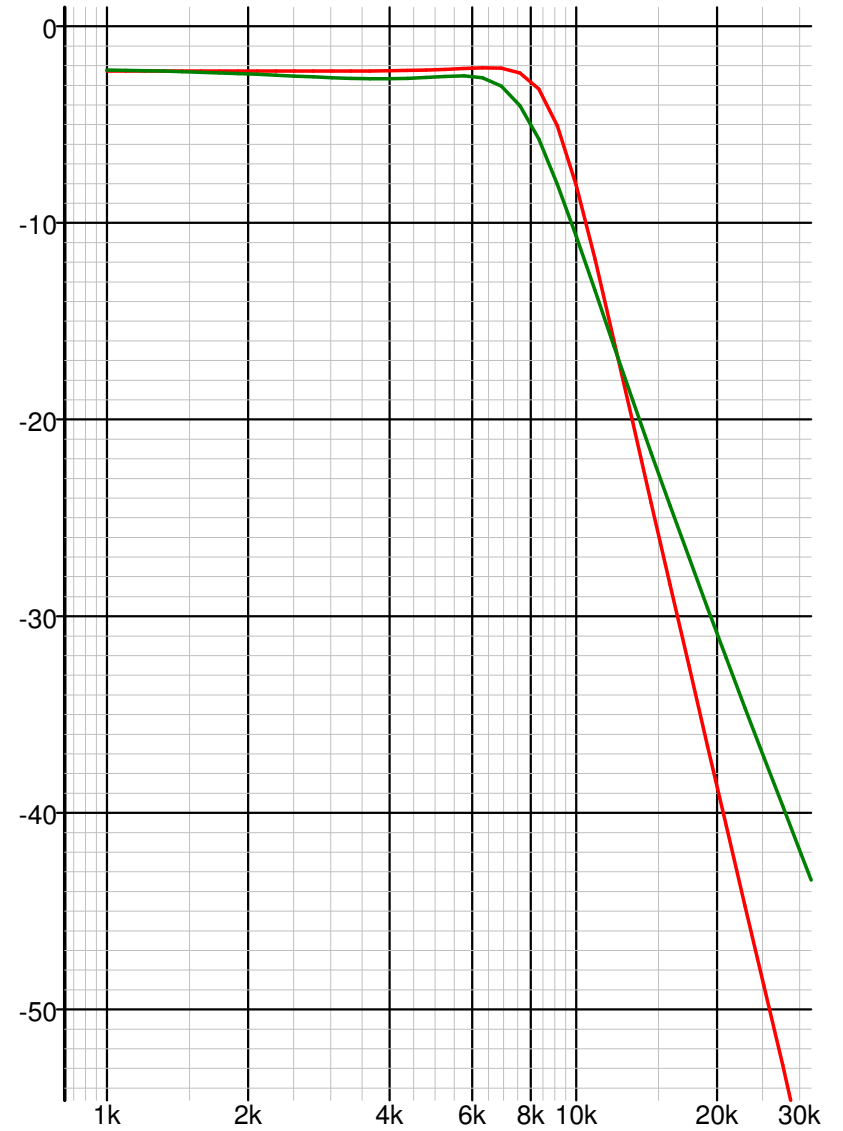

Frequency / Hertz